

# Assignment No.1

Surabhi Seetha

You can get all assembly codes here

<https://github.com/SurabhiSeetha/Fwciith2022/tree/main/Assignment%201/codes/asm>

You can get all python codes here

<https://github.com/SurabhiSeetha/Fwciith2022/tree/main/Assignment%201/codes/src>

You can get all avr gcc codes here

<https://github.com/SurabhiSeetha/Fwciith2022/tree/main/avr%20gcc>

and latex-tikz codes from

[https://github.com/SurabhiSeetha/Fwciith2022/blob/main/Assignment%201/\(Latex\).tex](https://github.com/SurabhiSeetha/Fwciith2022/blob/main/Assignment%201/(Latex).tex)

## 1 QUESTION-2015 SECTION C Q6(D)

Reduce the following Boolean Expression to its simplest form using k-map  $F(X, Y, Z, W) = \sum(0, 1, 6, 8, 9, 10, 11, 12, 15)$

**Abstract- This manual shows how to use 7447 BCD-seven segment display encoder to display Boolean Logic**

## 2 CONTENTS

Components	3
Hardware	4
Solution	5

## 3 COMPONENTS

Component	Value	Quantity
Resistor	220 Ohm	1
Arduino	UNO	1
Seven Segment Display		1
Decoder	7447	1
Jumper Wires	M-M	20
Breadboard		1

Table 3.0

## 4 HARDWARE

Make connections between seven segment display and the 7447 ic as per the given table

7447 pins	13	12	11	10	9	15	14
Display	a	b	c	d	e	f	g

Table 4.0

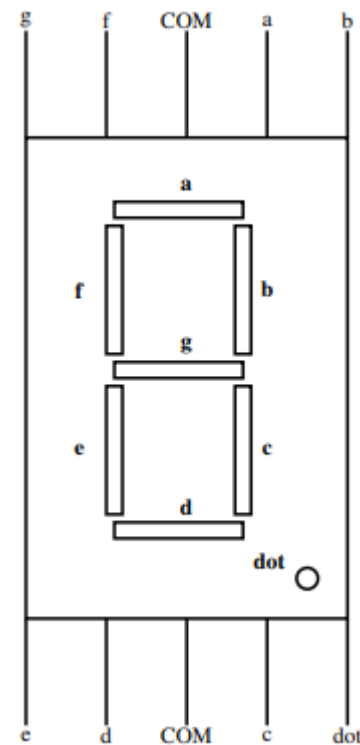


Figure 1

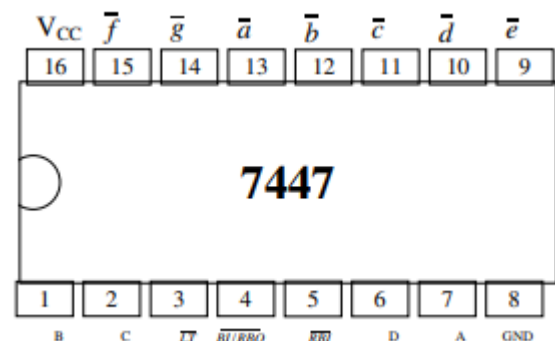


Figure 2

Make the connections from 7447 ic pins A,B,C,D onto the arduino board pins

<b>7447</b>	D	C	B	A
<b>Arduino</b>	5	4	3	2

Table 4.1

	X	Y	Z	W
<b>Input</b>	0	1	1	0
<b>Arduino</b>	6	7	8	9

Table 4.2

In the above example we are taking number 6 as input to arduino,so the connections are made accordingly by giving it to 0 which is ground and 1 to the input.

## 5 SOLUTION

### Truth Table

X	Y	Z	W	F(X,Y,Z,W)
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Table 5.0

XY \ ZW	00	01	11	10
00	1	1	0	0
01	0	0	0	1
11	1	0	1	0
10	1	1	1	1

Table 5.1

The expression from above k-map is  $XY'$

XY \ ZW	00	01	11	10
00	1	1	0	0
01	0	0	0	1
11	1	0	1	0
10	1	1	1	1

Table 5.2

The expression from above k-map is  $XZ'W'$

XY \ ZW	00	01	11	10
00	1	1	0	0
01	0	0	0	1
11	1	0	1	0
10	1	1	1	1

Table 5.3

The expression from above k-map is  $XZW$

XY \ ZW	00	01	11	10
00	1	1	0	0
01	0	0	0	1
11	1	0	1	0
10	1	1	1	1

Table 5.4

The expression from above k-map is  $Y'Z'$

XY \ ZW	00	01	11	10
00	1	1	0	0
01	0	0	0	1
11	1	0	1	0
10	1	1	1	1

Table 5.5

The expression from above k-map is  $XYZW'$

1. By solving the expression in Table 5.1, we get our first term as  $XY'$
2. By solving Table 5.2 we get the second term as  $XZ'W'$
3. By solving the k-map in Table 5.3, we get the third term as  $XZW$
4. By Solving Table 5.3 we get the fourth term as  $Y'Z'$
5. Finally for the last term, we get the term from the Table 5.5 as  $X'YZW'$

$$F = XY' + XZ'W' + XZW + Y'Z' + X'YZW'$$